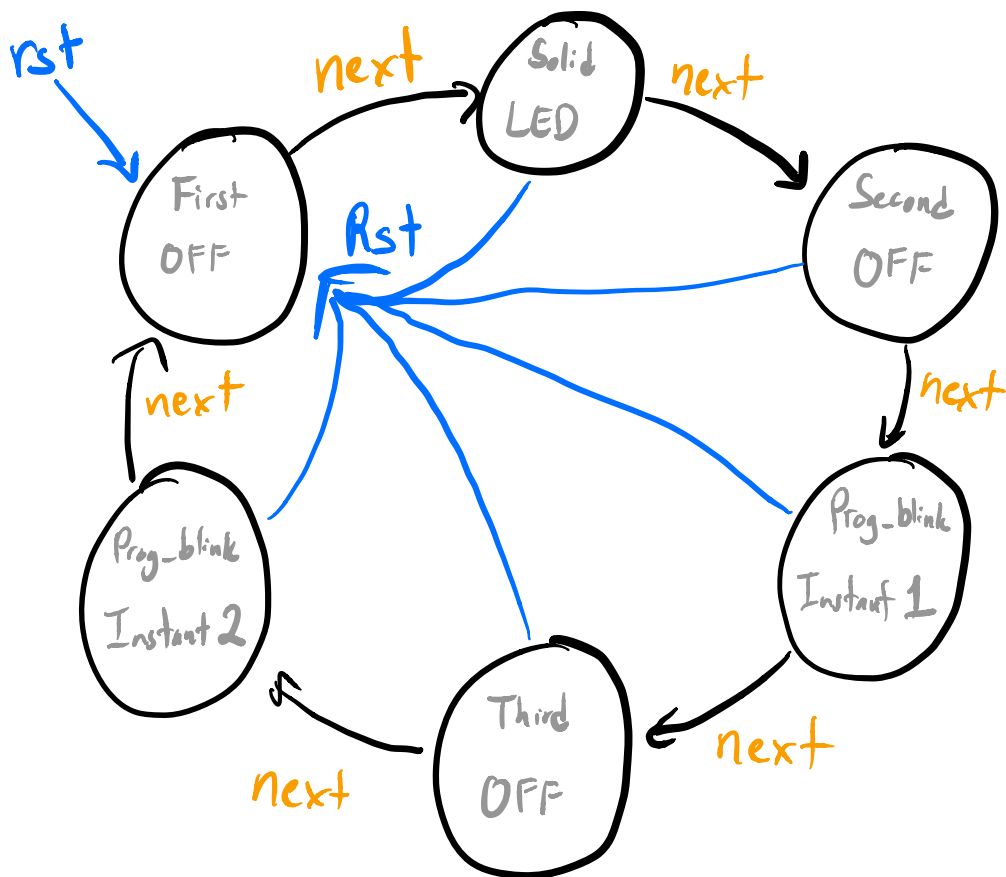



LAB 3

Julia Wang
Tristan Abarca
Troy Lawrence


3. Diagrams Master FSM




Shifter

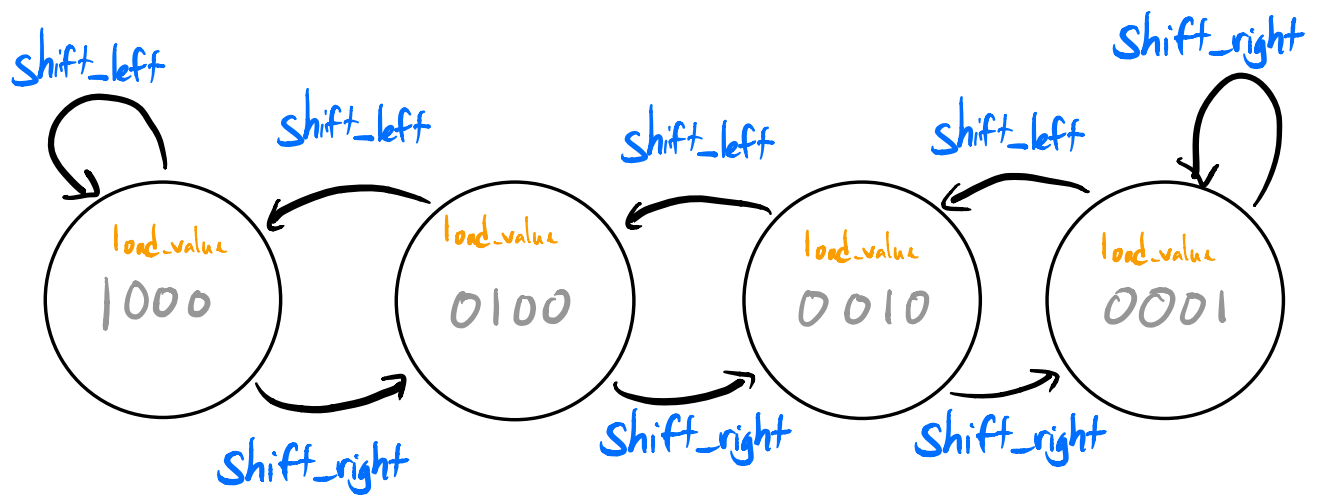


Blinker

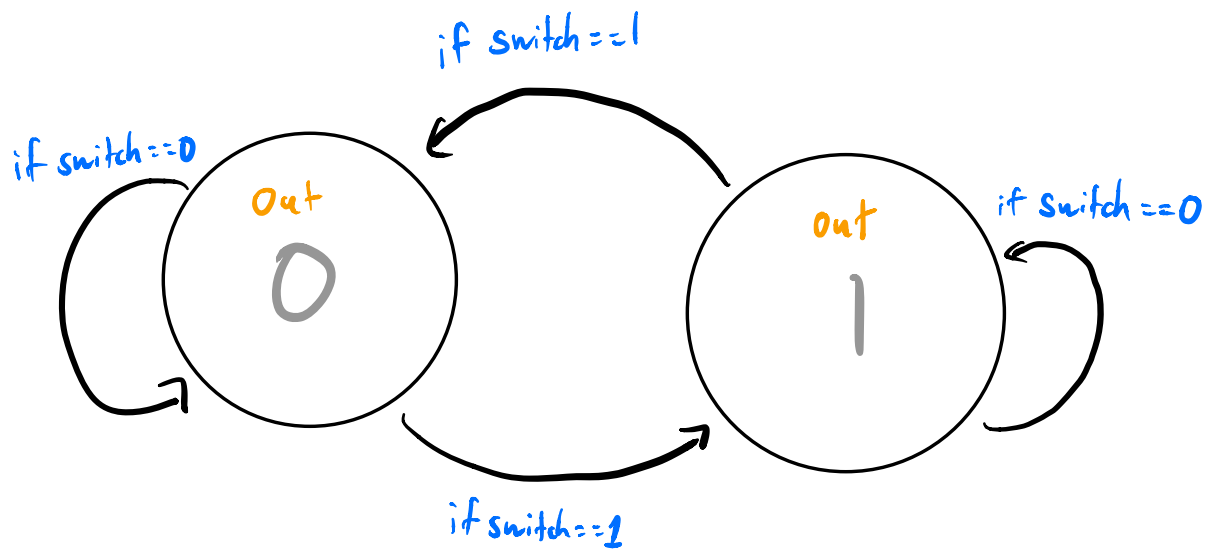

Timer

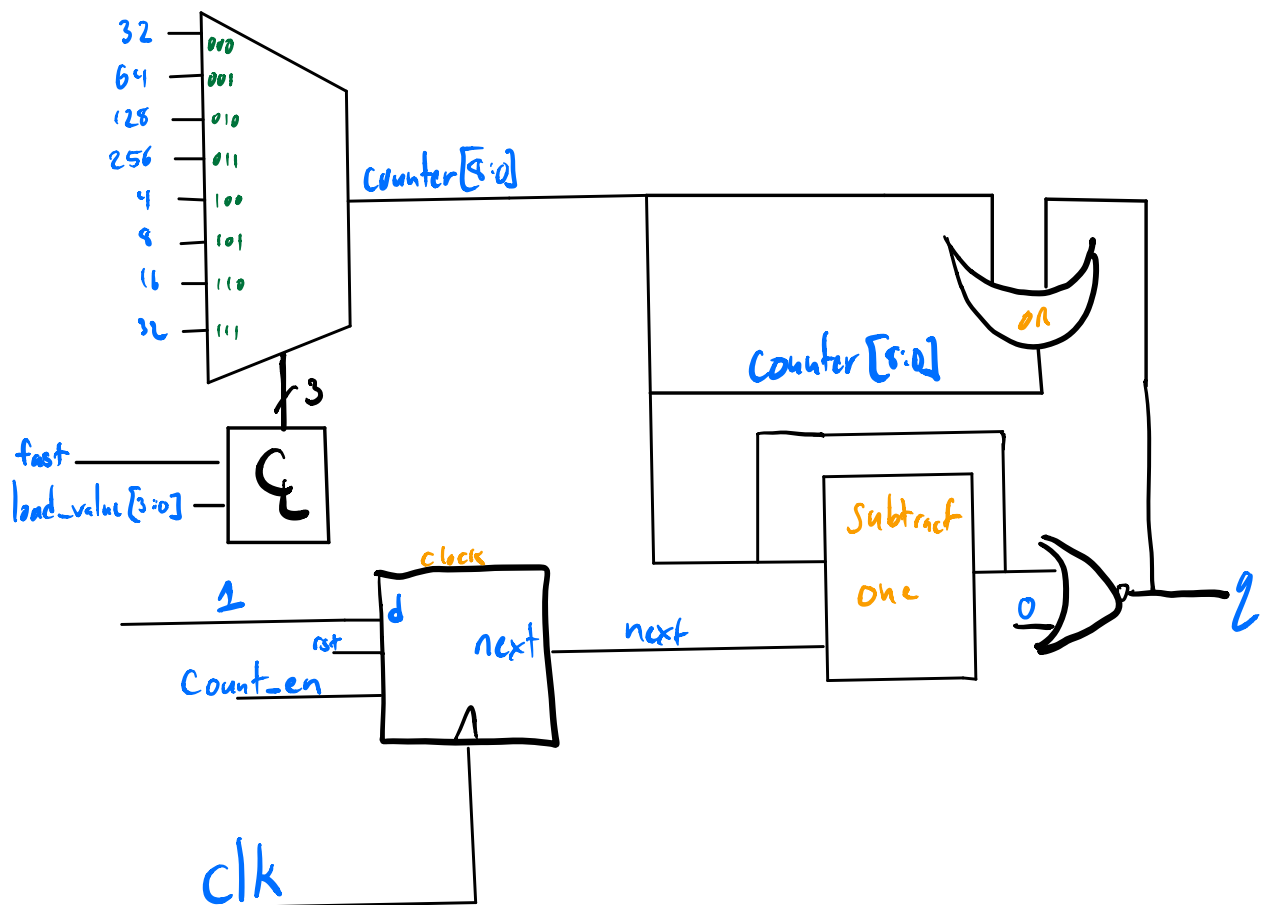

Beat 32

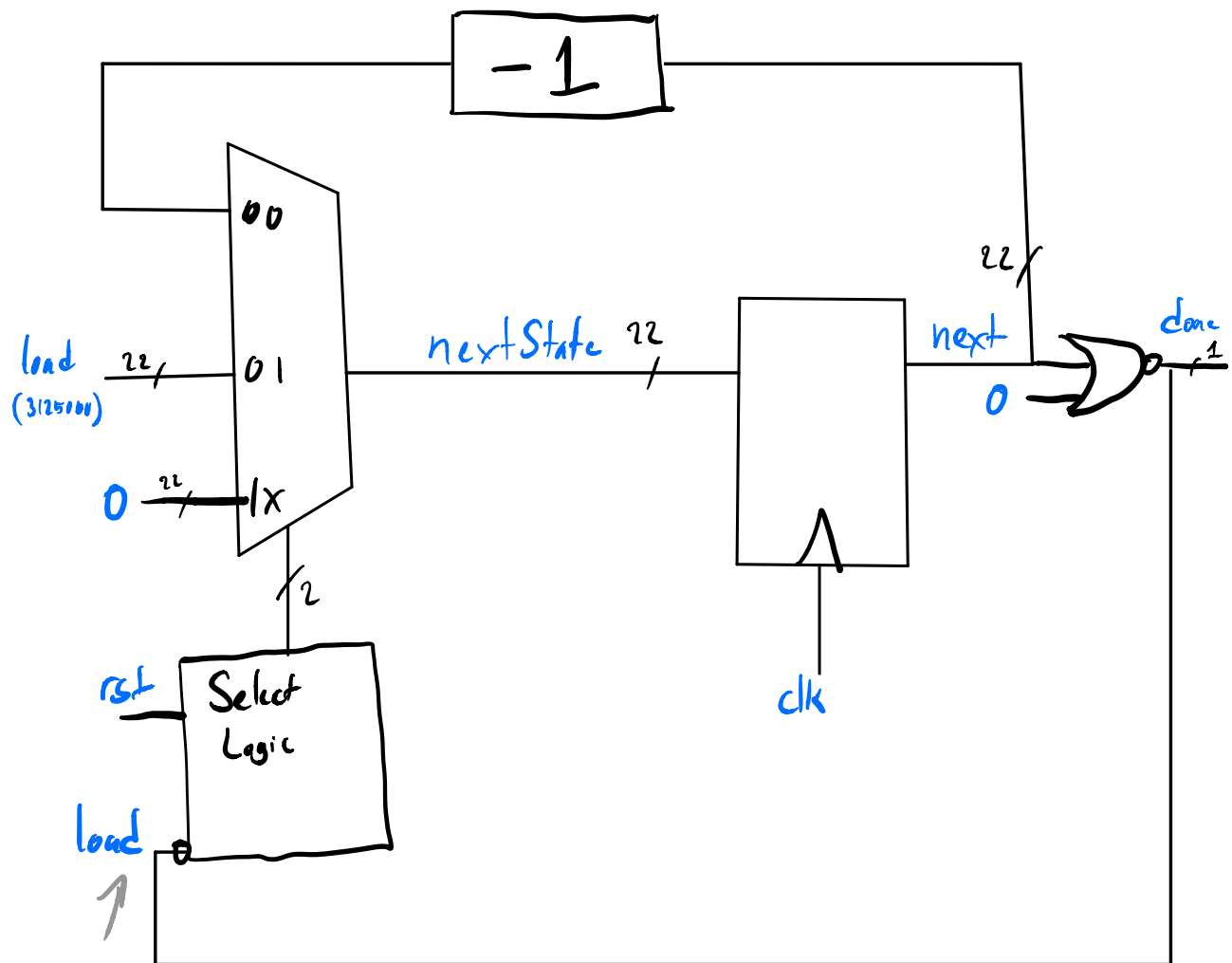

is on
when done == 0